

Assignment 7: Sympy

Chollangi Dheeraj Sai [EE20B029]

April 8, 2022

1 Overview

In this assignment, the focus will be on two powerful capabilities of Python:

1. Symbolic Algebra
2. Analysis of Circuits using Laplace Transforms

With the help of the sympy module, we will analyse some circuit models

2 Lowpass filter

The low pass filter that we use gives the following matrix equation after simplification of the modified nodal equations.

$$\begin{pmatrix} 0 & 0 & 1 & -\frac{1}{G} \\ -\frac{1}{1+sR_2C_2} & 1 & 0 & 0 \\ 0 & -G & G & 1 \\ -\frac{1}{R_1} - \frac{1}{R_2} - sC_1 & \frac{1}{R_2} & 0 & sC_1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_p \\ V_m \\ V_o \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ -V_i(s)/R_1 \end{pmatrix}$$

The python code used is as follows

```
def lowpass(R1, R2, C1, C2, G, Vi):
    s = symbols("s")
    A = Matrix(
        [
            [0, 0, 1, -1 / G],
            [-1 / (1 + s * R2 * C2), 1, 0, 0],
            [0, -G, G, 1],
            [-(1 / R1) - (1 / R2) - (s * C1), 1 / R2, 0, s * C1],
        ]
    )
    b = Matrix([0, 0, 0, -Vi / R1])
    V = A.inv() * b
    return (A, b, V)
```

The magnitude and phase bode plots of this filter are shown below.

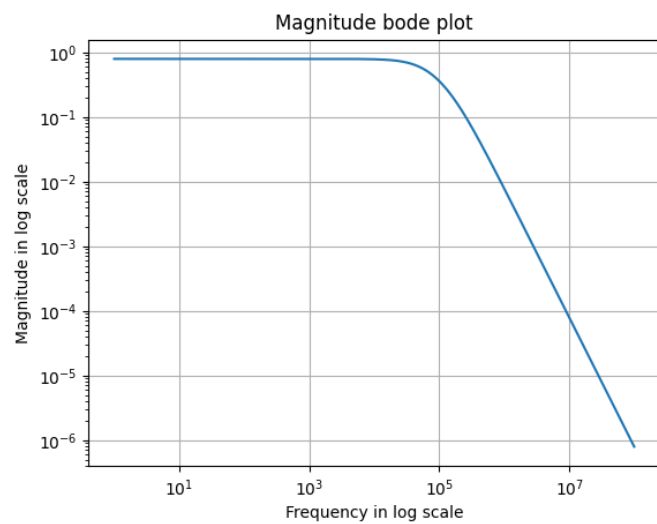


Figure 1: Magnitude bode plot


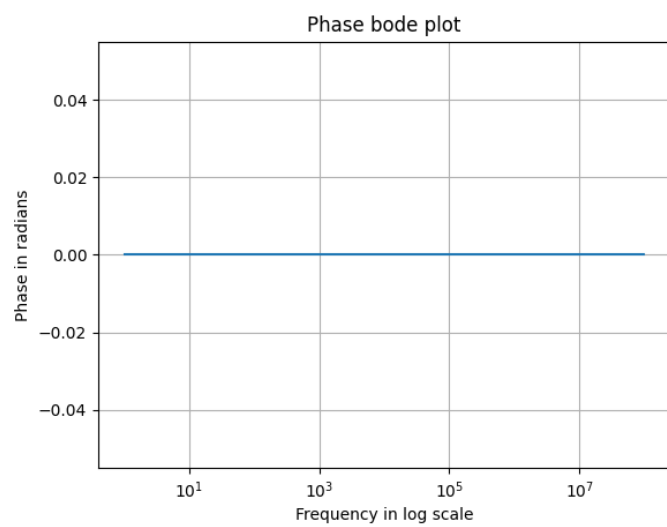
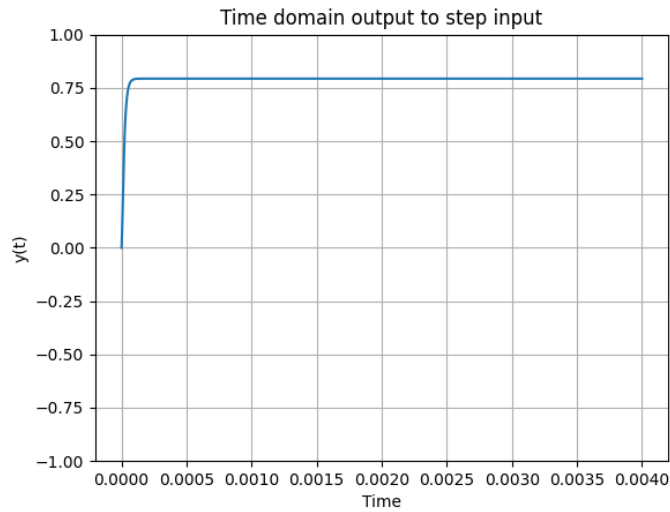


Figure 2: Phase bode plot

3 Step response of lowpass filter

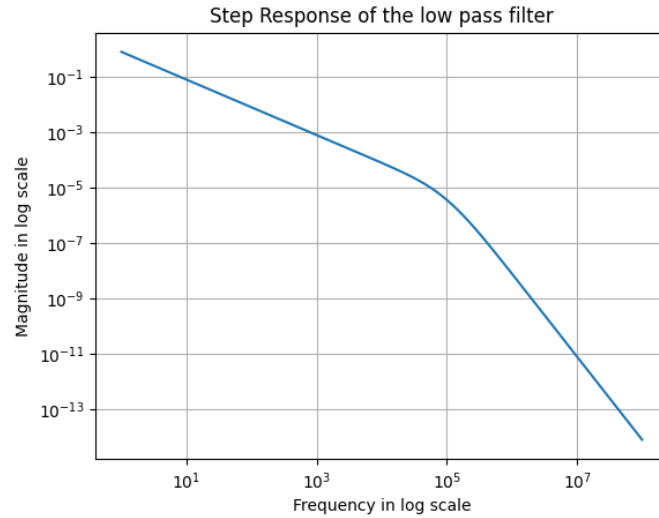An input step is passed into the lowpass filter, the response is calculated. We are plotting the response in both frequency domain and time domain. They are shown below



4 Lowpass filter output for sinusoidal input

Let us now analyse what will happen if we pass a sinusoidal signal into a lowpass filter. We will analyse the output by plotting its curve in time domain. The plot of the input sinusoid is as shown below:

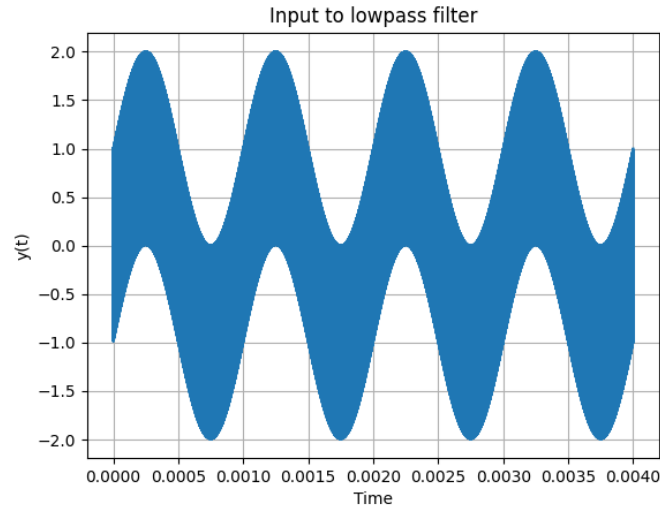


Figure 3: Input sinusoid

The output of the lowpass filter when the above sinusoid is passed through it is plotted below:

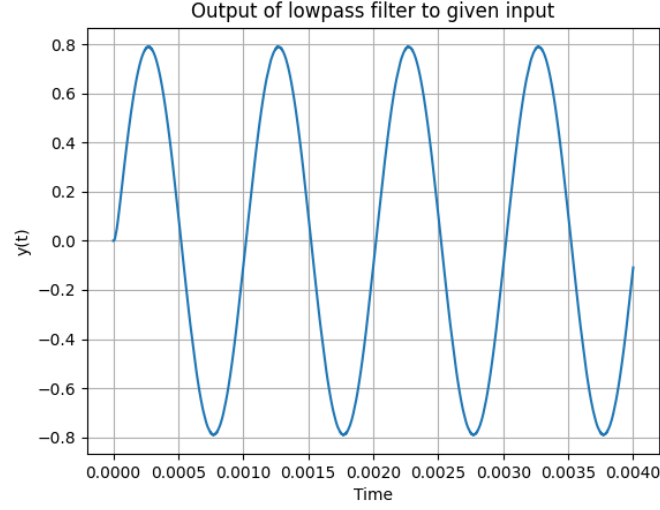


Figure 4: Lowpass filter output

5 Highpass filter

The high pass filter is modelled by solving the below matrix equation. This matrix is a direct consequence of the nodal equations of high pass filter.

$$\begin{pmatrix} 0 & 0 & 1 & -\frac{1}{G} \\ -\frac{sR_3C_2}{1+sR_3C_2} & 1 & 0 & 0 \\ 0 & -G & G & 1 \\ -1 - (sR_1C_1) - (sR_3C_2) & sC_2R_1 & 0 & 1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_p \\ V_m \\ V_o \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ -V_i(s)sR_1C_1 \end{pmatrix}$$

The python code snippet that declares the high pass function and solves the matrix equation to get the V matrix is as shown below:

```
def highpass(R1, R3, C1, C2, G, Vi):
    s = symbols("s")
    A = Matrix(
        [
            [0, 0, 1, -1 / G],
            [-(s * R3 * C2) / (1 + s * R3 * C2), 1, 0, 0],
            [0, -G, G, 1],
            [-(s * C1) - (s * C2) - (1 / R1), s * C2, 0, 1 / R1],
        ]
    )
    b = Matrix([0, 0, 0, -Vi * s * C1])
    V = A.inv() * b
    return (A, b, V)
```

The magnitude and phase bode plots of this filter are as shown below:

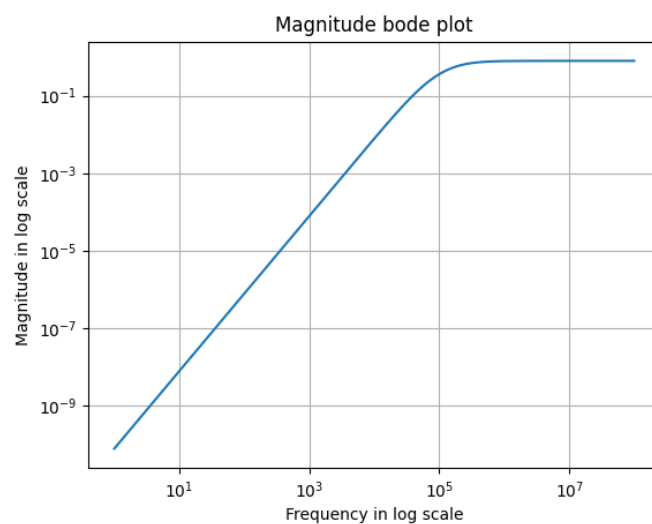


Figure 5: Magnitude bode plot


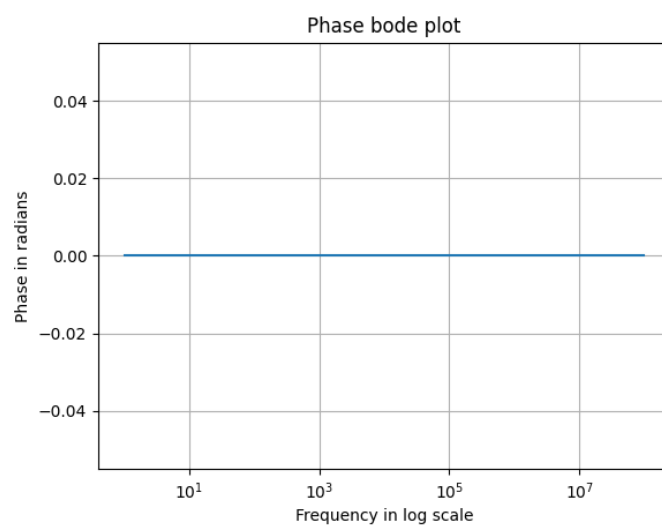
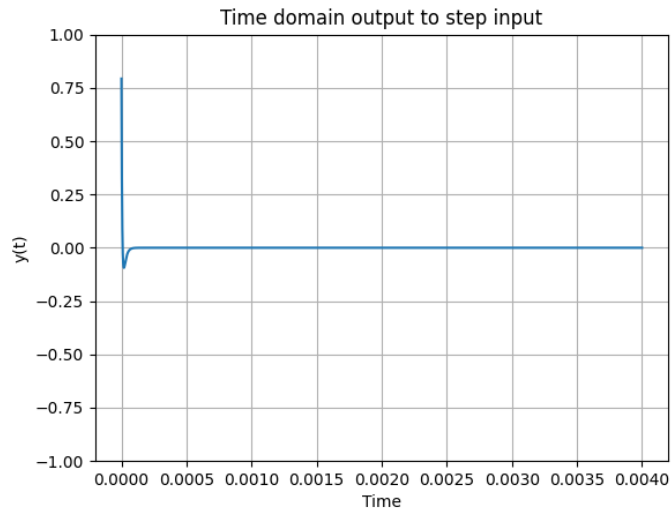


Figure 6: Phase bode plot

6 Step response of highpass filter

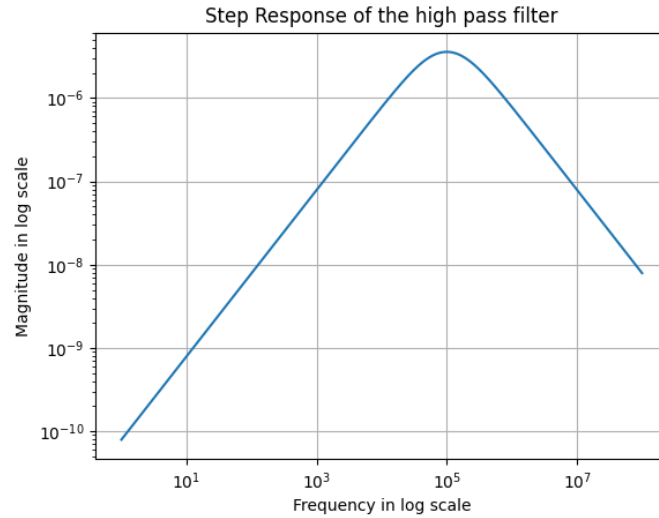An input step is passed into the highpass filter, the response is calculated. We are plotting the response in both frequency domain and time domain. They are shown below



7 Highpass filter output for sinusoidal input

Let us now analyse what will happen if we pass a sinusoidal signal into a high filter. We will analyse the output by plotting its curve in time domain.

The output of the highpass filter when the sinusoid is passed through it is plotted below:

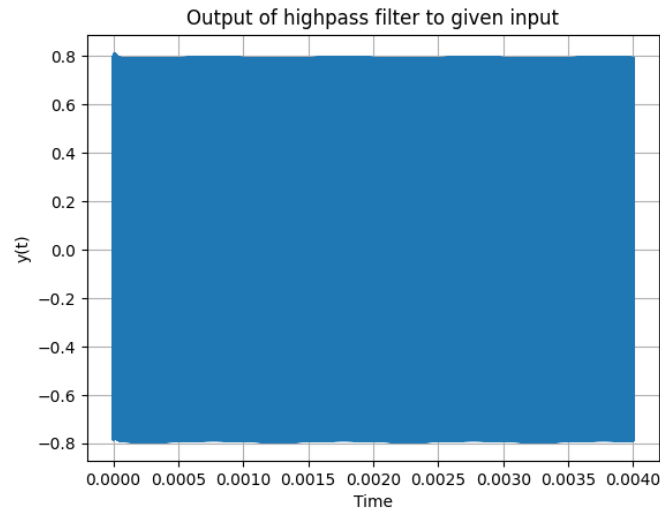


Figure 7: Highpass filter output

8 Highpass filter output for a decaying sinusoid

We wish to analyse the output of the highpass filter when we pass a signal which is a decaying sinusoid. We will analyse the behaviour of this highpass filter for different frequencies of the input decaying sinusoid. Let us consider the below sinusoid and pass it into the highpass filter.

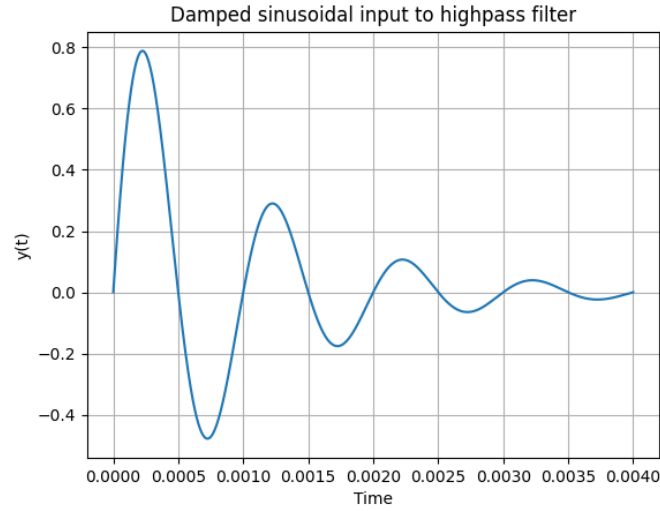


Figure 8: Low frequency decaying sinusoid

The output obtained from the filter is as follows.

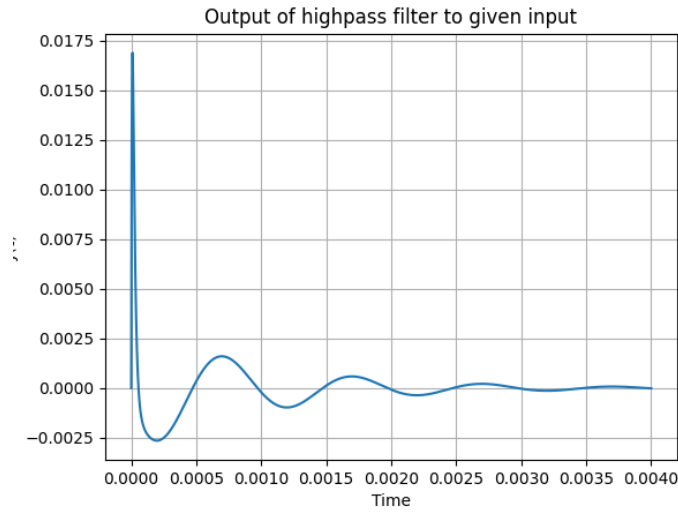


Figure 9: Highpass filter output

. Let us now pass another sinusoid into the filter. Its plot is shown below.

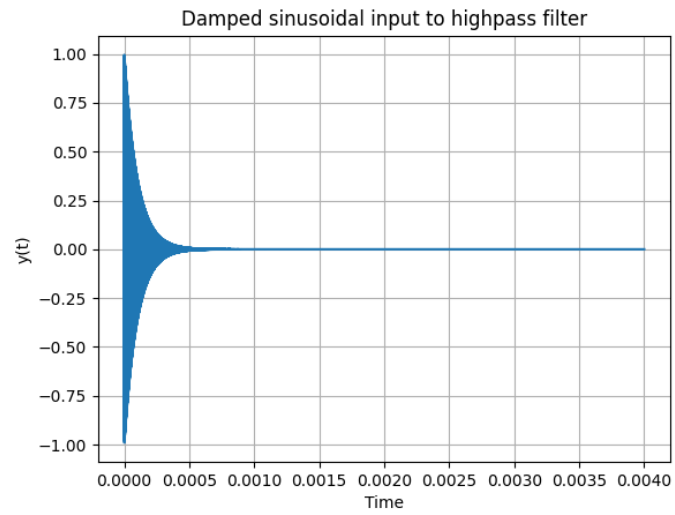


Figure 10: High frequency decaying sinusoid

The output in this case is as follows:

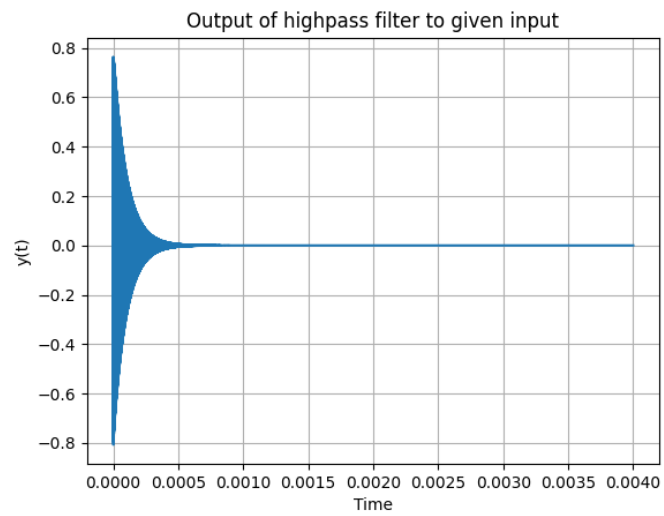


Figure 11: Highpass filter output

9 Conclusion

We can conclude that sympy module has allowed us to analyse quite complicated circuits by analytically solving their nodal equations using matrices. Sympy allowed us to use variables for defining new constants, which made it easier to study the circuits. We then interpreted the solutions by plotting time domain responses using the signals toolbox. Thus, sympy combined with the scipy.signal module is a very useful toolbox for analyzing complicated systems like the active filters in this assignment.